

COSE222: Computer Architecture

Ch. 4 The Processor (The Single-Cycle Processor)

Gunjae Koo

Department of Computer Science and Engineering
Korea University



KOREA
UNIVERSITY

* Based on the lecture slides from “Computer Organization and Design”


Introduction

- CPU performance factors
 - Instruction count
 - Determined by ISA and compiler
 - CPI and Cycle time
 - Determined by CPU hardware
- We will examine two RISC-V implementations
 - A simplified version
 - A more realistic pipelined version
- Simple subset, shows most aspects
 - Memory reference: `ld`, `sd`
 - Arithmetic/logical: `add`, `sub`, `and`, `or`
 - Control transfer: `beq`

Instruction Execution


- PC → instruction memory, fetch instruction
- Register numbers → register file, read registers
- Depending on instruction class
 - Use ALU to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch comparison
 - Access data memory for load/store
 - $PC \leftarrow \text{target address or } PC + 4$

CPU Overview

 


Multiplexers (MUXes)

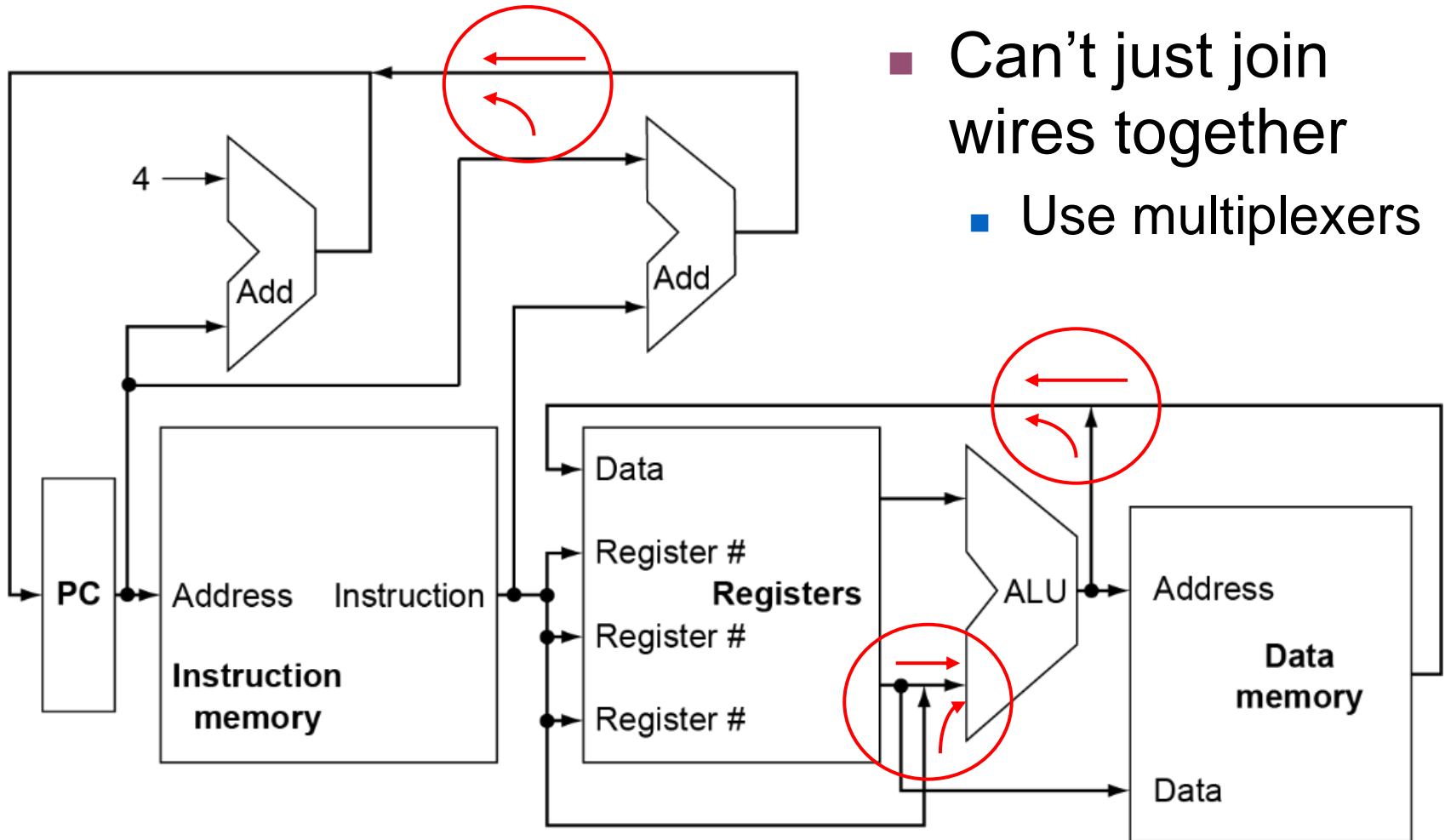- Can't just join wires together
 - Use multiplexers



Control

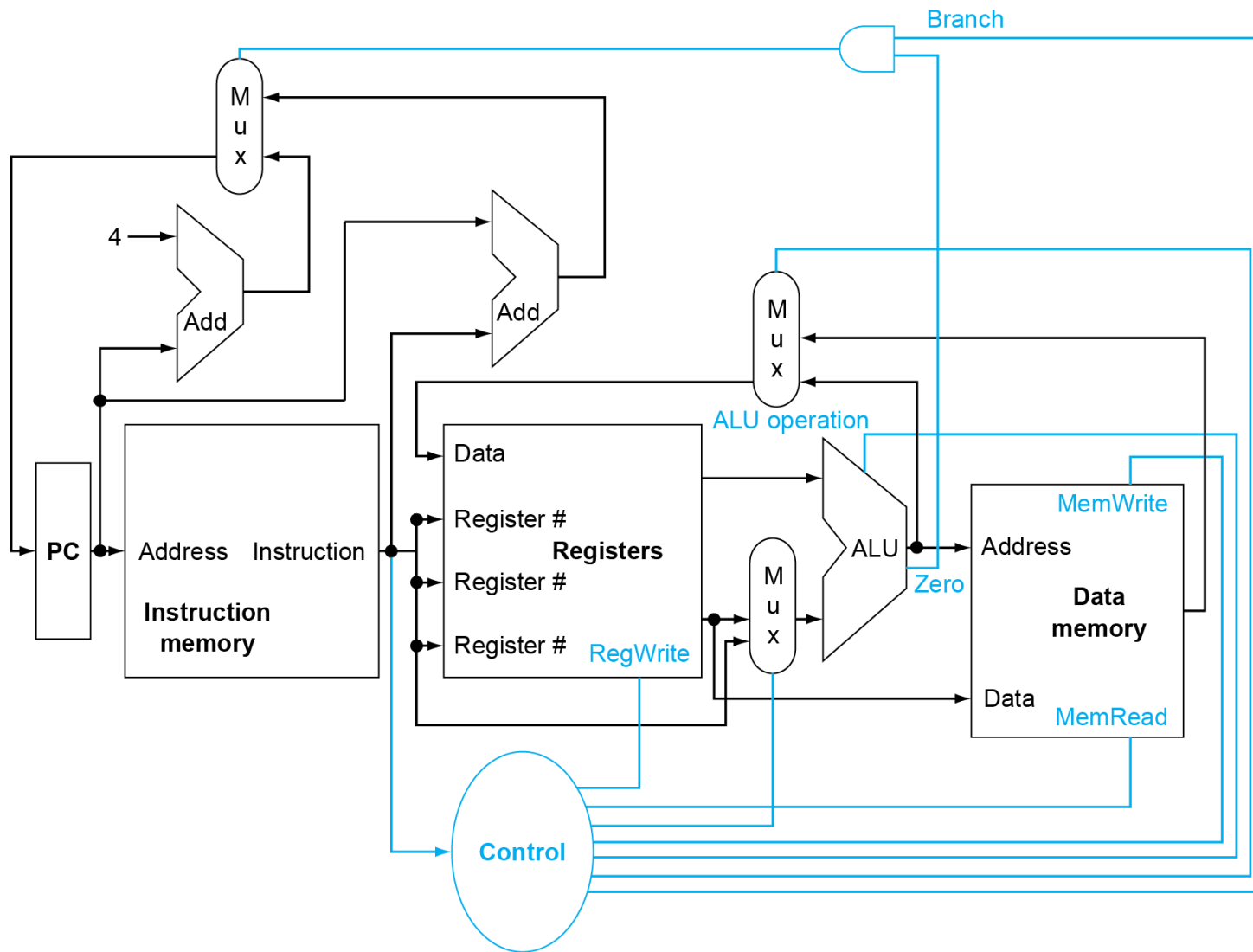


Logic Design Conventions

- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information

Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 


- Adder

- $Y = A + B$

 



- Arithmetic/Logic Unit

- $Y = F(A, B)$

 



Sequential Elements

  - Register: stores data in a circuit
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1




Sequential Elements

  - Register with write control
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Clocking Methodology

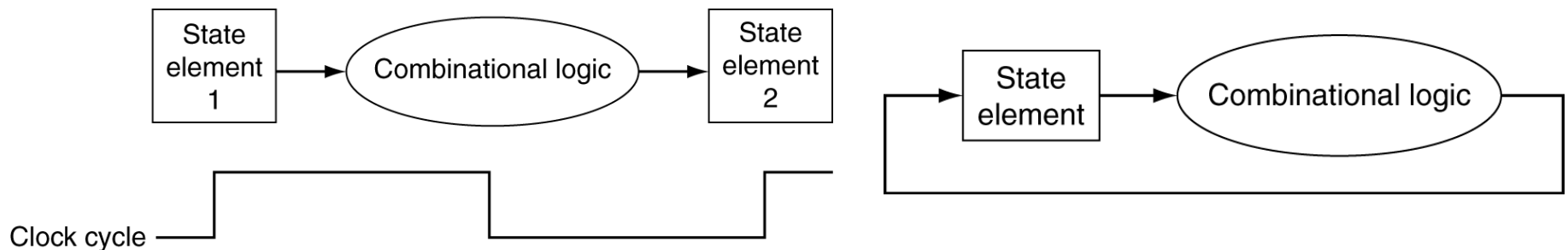
- Combinational logic transforms data during clock cycles
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period



Building a Datapath


- Datapath
 - Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will build a RISC-V datapath incrementally
 - Refining the overview design

Instruction Fetch

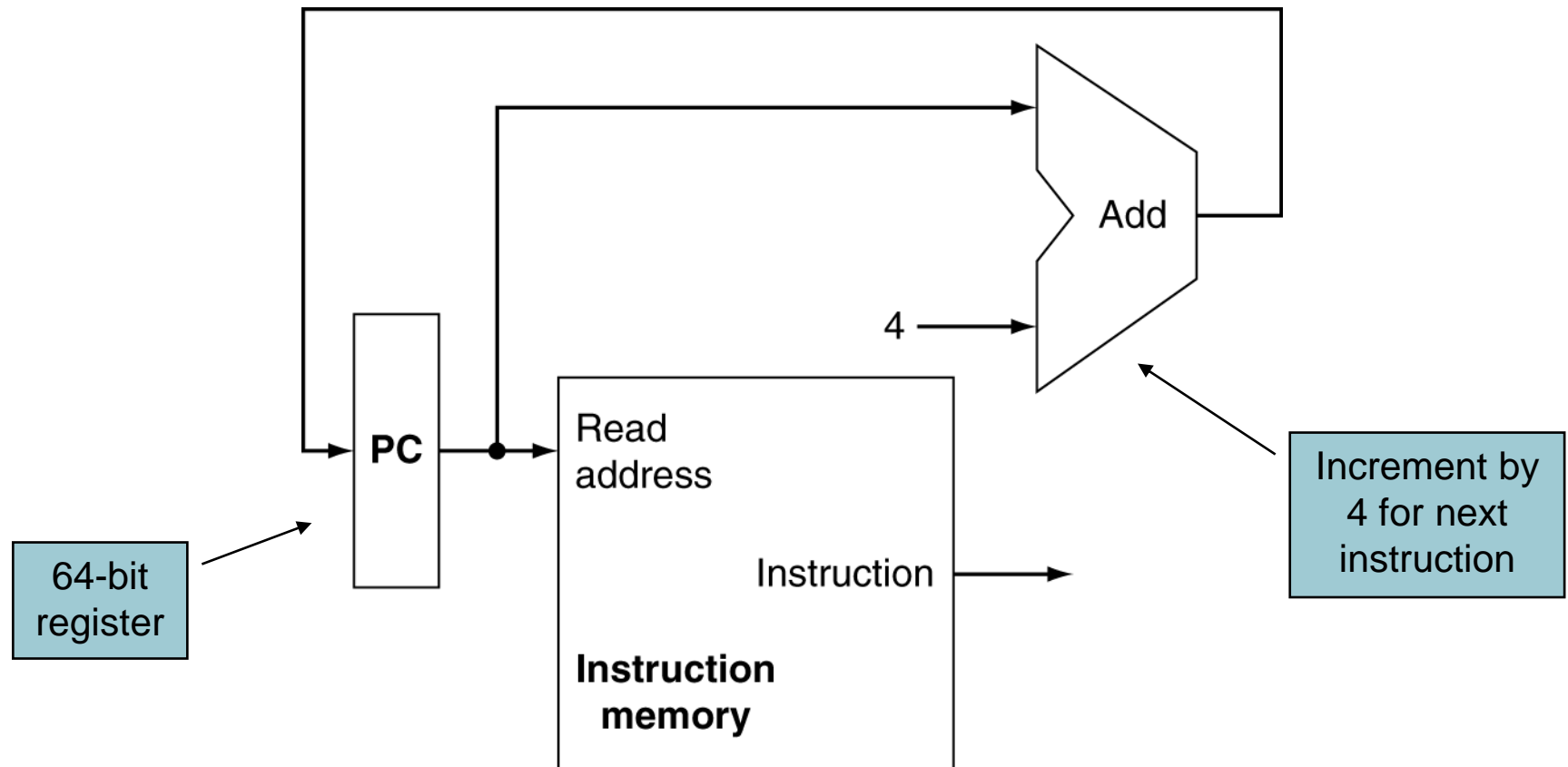


R-Format Instructions

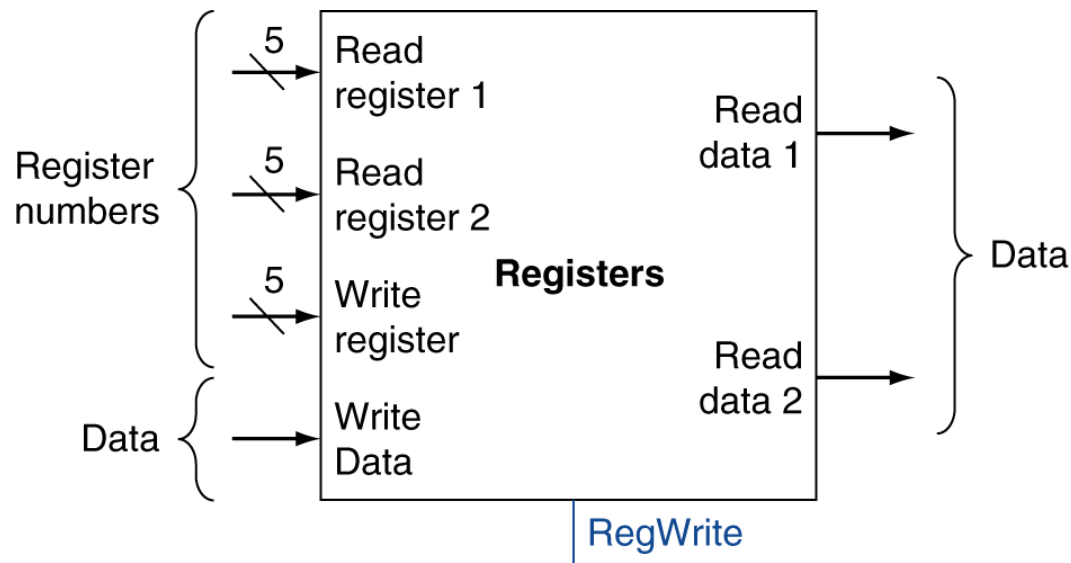- Read two register operands
- Perform arithmetic/logical operation
- Write register result



a. Registers

 

b. ALU

RISC-V R-format Instructions (*review*)




■ Instruction fields


- opcode: operation code
- rd: destination register number
- funct3: 3-bit function code (additional opcode)
- rs1: the first source register number
- rs2: the second source register number
- funct7: 7-bit function code (additional opcode)

Load/Store Instructions

 - Read register operands
- Calculate address using 12-bit offset
 - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory




a. Data memory unit

 

b. Immediate generation unit

RISC-V I-format Instructions (*review*)

 


- Immediate arithmetic and load instructions
 - rs1: source or base address register number
 - immediate: constant operand, or offset added to base address
 - 2s-complement, sign extended

Branch Instructions

- Read register operands
- Compare operands
 - Use ALU, subtract and check Zero output
- Calculate target address
 - Sign-extend displacement
 - Shift left 1 place (halfword displacement)
 - Add to PC value


Branch Instructions

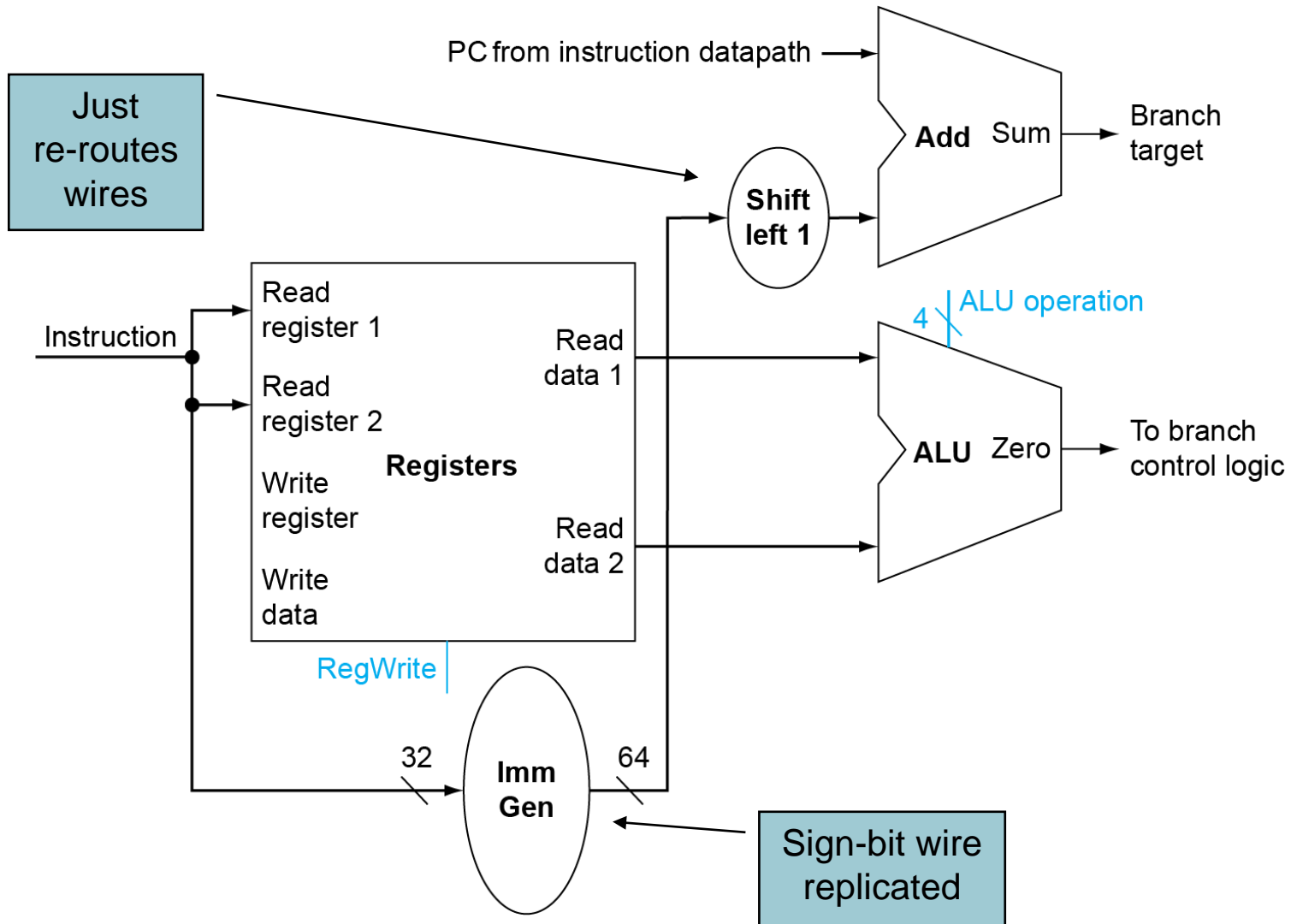


Composing the Elements

- First-cut data path does an instruction in one clock cycle
 - Each datapath element can only do one function at a time
 - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions

R-Type/Load/Store Datapath

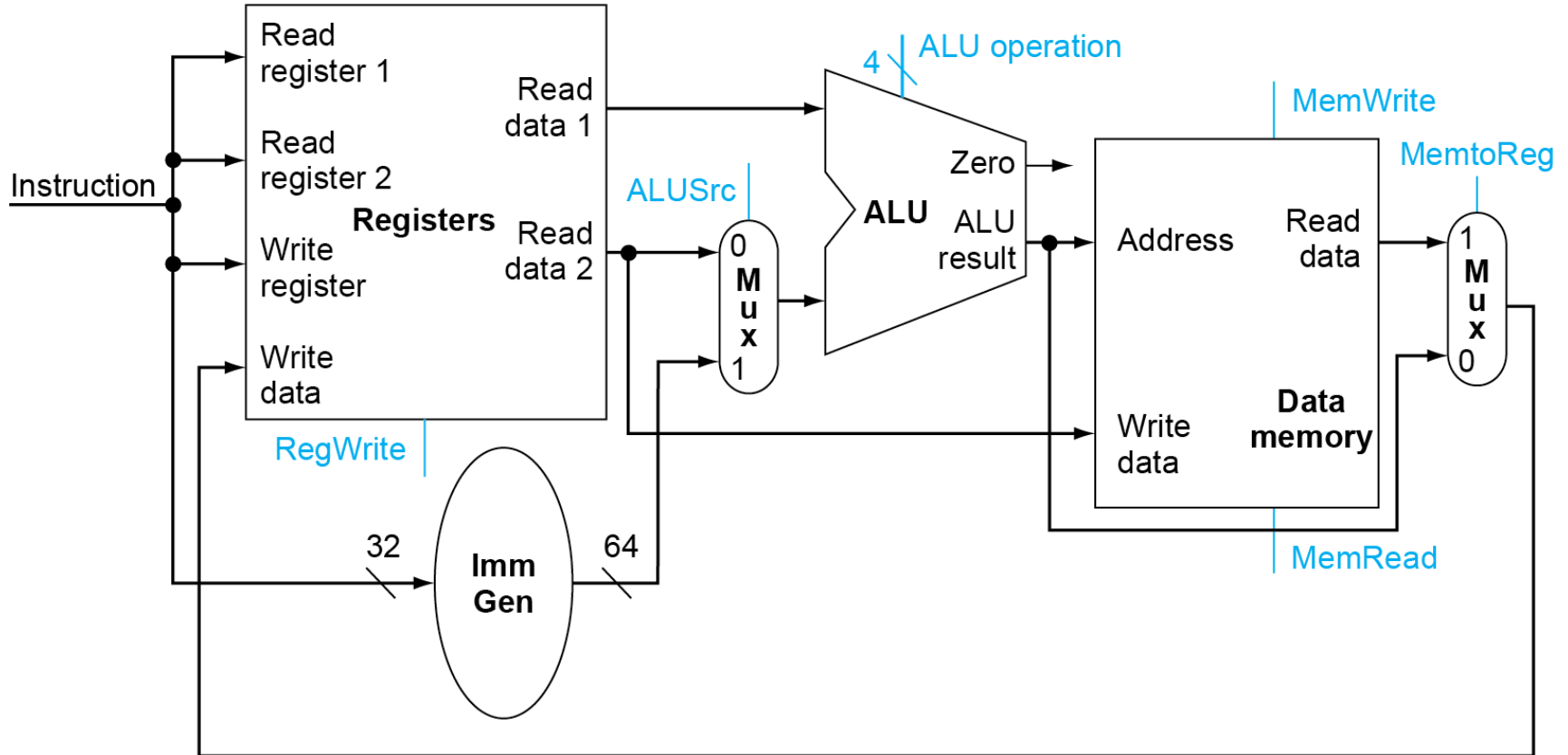

Full Datapath

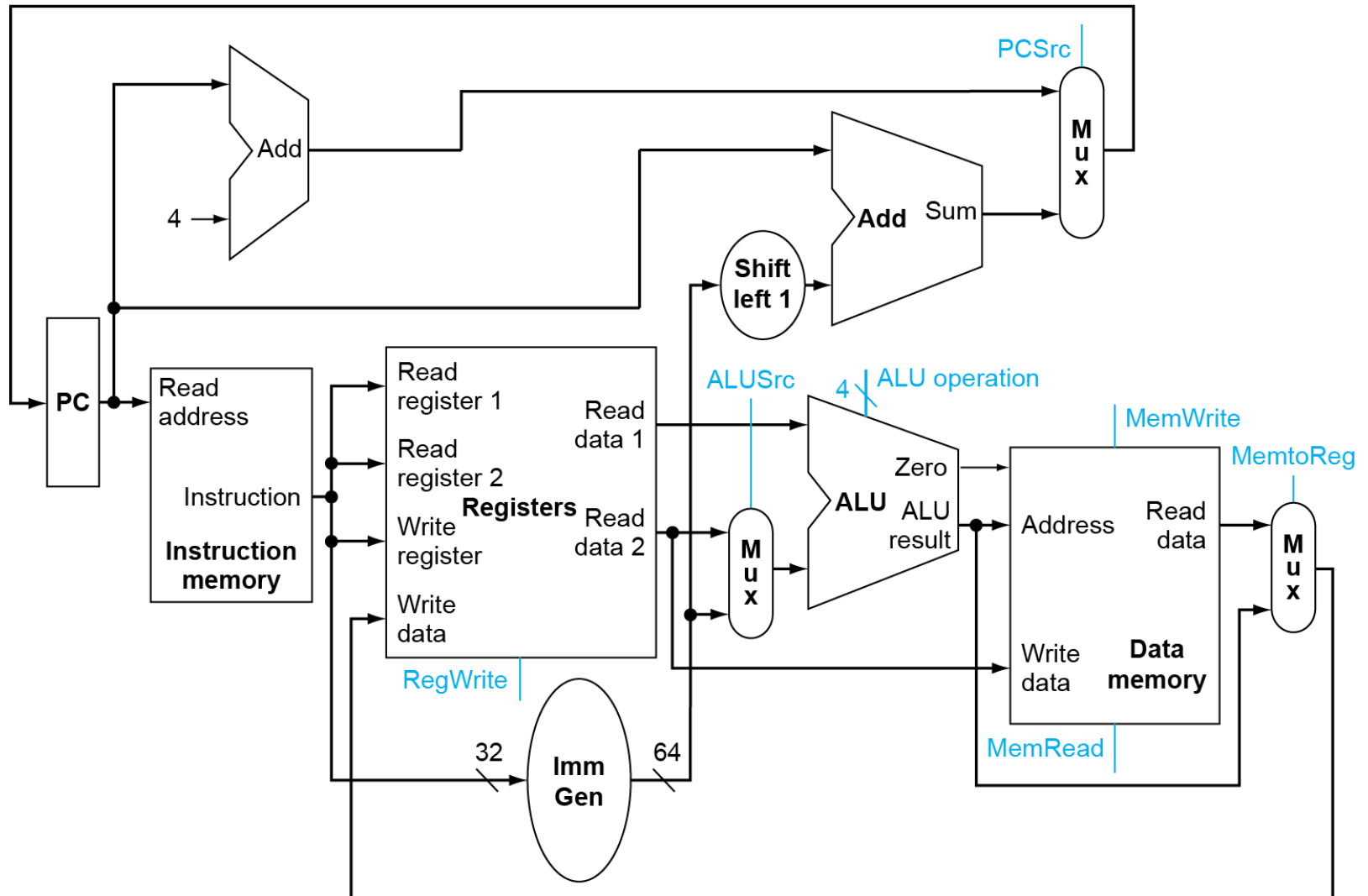

A Simple Implementation Scheme

ALU Control

- ALU used for
 - Load/Store: F = add
 - Branch: F = subtract
 - R-type: F depends on opcode

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract

ALU Control

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

opcode	ALUOp	Operation	Opcode field	ALU function	ALU control
ld	00	load register	0000011	add	0010
sd	00	store register	0100011	add	0010
beq	01	branch on equal	1100011	subtract	0110
R-type	10	add	0110011	add	0010
		subtract		subtract	0110
		AND		AND	0000
		OR		OR	0001

The Main Control Unit

■ Control signals derived from instruction


Name (Bit position)	Fields					
	31:25	24:20	19:15	14:12	11:7	6:0
(a) R-type	funct7	rs2	rs1	funct3	rd	opcode
(b) I-type	immediate[11:0]		rs1	funct3	rd	opcode
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode

ALUOp		Funct7 field							Funct3 field			Operation
ALUOp1	ALUOp0	I[31]	I[30]	I[29]	I[28]	I[27]	I[26]	I[25]	I[14]	I[13]	I[12]	
0	0	X	X	X	X	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	X	X	X	X	0110
1	X	0	0	0	0	0	0	0	0	0	0	0010
1	X	0	1	0	0	0	0	0	0	0	0	0110
1	X	0	0	0	0	0	0	0	1	1	1	0000
1	X	0	0	0	0	0	0	0	1	1	0	0001


Control Unit (RV32I)

Base interger instrucionts: RV32I, register width = 32									
Category	Mnemonic	Instrunction		Format	Name	Description (in Verilog)	opcode	func3	func7
Loads	LB	LB	rd, rs1, imm	I	Load Byte	$R[rd] = \{24'bM[]\}(7), M[R[rs1]+imm](7:0)\}$	0000011	000	
	LH	LH	rd, rs1, imm	I	Load Halfword	$R[rd] = \{16'bM[]\}(15), M[R[rs1]+imm](15:0)\}$	0000011	001	
	LW	LW	rd, rs1, imm	I	Load Word	$R[rd] = M[R[rs1]+imm]$	0000011	010	
	LBU	LBU	rd, rs1, imm	I	Load Byte Unsigned	$R[rd] = \{24'b0, M[R[rs1]+imm](7:0)\}$	0000011	100	
	LHU	LHU	rd, rs1, imm	I	Load Halfwaod Unsigned	$R[rd] = \{16'b0, M[R[rs1]+imm](15:0)\}$	0000011	101	
Stores	SB	SB	rs1, rs2, imm	S	Store Byte	$M[R[rs1]+imm](7:0) = R[rs2](7:0)$	0100011	000	
	SH	SH	rs1, rs2, imm	S	Store Halfword	$M[R[rs1]+imm](15:0) = R[rs2](15:0)$	0100011	001	
	SW	SW	rs1, rs2, imm	S	Store Word	$M[R[rs1]+imm](31:0) = R[rs2](31:0)$	0100011	010	
Shifts	SLL	SLL	rd, rs1, rs2	R	Shift Left	$R[rd] = R[rs1] \ll R[rs2]$	0110011	001	0000000
	SLLI	SLLI	rd, rs1, shamt	I	Shift Left Immediate	$R[rd] = R[rs1] \ll imm$	0010011	001	0000000
	SRL	SRL	rd, rs1, rs2	R	Shift Right	$R[rd] = R[rs1] \gg R[rs2]$	0110011	101	0000000
	SRLI	SRLI	rd, rs1, shamt	I	Shift Right Immediate	$R[rd] = R[rs1] \gg imm$	0010011	101	0000000
	SRA	SRA	rd, rs1, rs2	R	Shift Right Arithmetic	$R[rd] = R[rs1] \gg R[rs2] \text{ (arithmetic)}$	0110011	101	0100000
	SRAI	SRAI	rd, rs1, shamt	I	Shift Right Arith Imm	$R[rd] = R[rs1] \gg imm \text{ (arithmetic)}$	0010011	101	0100000
Arithmetic	ADD	ADD	rd, rs1, rs2	R	Add	$R[rd] = R[rs1] + R[rs2]$	0110011	000	0000000
	ADDI	ADDI	rd, rs1, imm	I	Add Immediate	$R[rd] = R[rs1] + imm$	0010011	000	
	SUB	SUB	rd, rs1, rs2	R	Subtract	$R[rd] = R[rs1] - R[rs2]$	0110011	000	0100000
	LUI	LUI	rd, imm	U	Load Upper Immediate	$R[rd] = \{imm, 12'b0\}$	0110111		
	AUIPC	AUIPC	rd, imm	U	Add Upper Imm to PC	$R[rd] = PC + \{imm, 12'b0\}$	0010111		
Logical	XOR	XOR	rd, rs1, rs2	R	XOR	$R[rd] = R[rs1] \wedge R[rs2]$	0110011	100	0000000
	XORI	XORI	rd, rs1, imm	I	XOR Immediate	$R[rd] = R[rs1] \wedge imm$	0010011	100	
	OR	OR	rd, rs1, rs2	R	OR	$R[rd] = R[rs1] \vee R[rs2]$	0110011	110	0000000
	ORI	ORI	rd, rs1, imm	I	OR Immediate	$R[rd] = R[rs1] \vee imm$	0010011	110	
	AND	AND	rd, rs1, rs2	R	AND	$R[rd] = R[rs1] \& R[rs2]$	0110011	111	0000000
	ANDI	ANDI	rd, rs1, imm	I	AND Immediate	$R[rd] = R[rs1] \& imm$	0010011	111	
Compare	SLT	SLT	rd, rs1, rs2	R	Set Less Than	$R[rd] = (R[rs1] < R[rs2]) ? 1: 0$	0110011	010	0000000
	SLTI	SLTI	rd, rs1, imm	I	Set Less Than Immediate	$R[rd] = (R[rs1] < imm) ? 1: 0$	0010011	010	
	SLTU	SLTU	rd, rs1, rs2	R	Set Less Than Unsigned	$R[rd] = (R[rs1] < R[rs2]) ? 1: 0 \text{ (unsigned)}$	0110011	011	0000000
	SLTIU	SLTIU	rd, rs1, imm	I	Set Less Than Imm Unsigned	$R[rd] = (R[rs1] < imm) ? 1: 0 \text{ (unsigned)}$	0010011	011	
Branches	BEQ	BEQ	rs1, rs2, imm	SB	Branch if Equal	if $(R[rs1] == R[rs2])$ $PC = PC + \{imm, 1'b0\}$	1100011	000	
	BNE	BNE	rs1, rs2, imm	SB	Branch if Not Equal	if $(R[rs1] != R[rs2])$ $PC = PC + \{imm, 1'b0\}$	1100011	001	
	BLT	BLT	rs1, rs2, imm	SB	Branch if Less Than	if $(R[rs1] < R[rs2])$ $PC = PC + \{imm, 1'b0\}$	1100011	100	
	BGE	BGE	rs1, rs2, imm	SB	Branch if Greater or Equal	if $(R[rs1] \geq R[rs2])$ $PC = PC + \{imm, 1'b0\}$	1100011	101	
	BLTU	BLTU	rs1, rs2, imm	SB	Branch if Less Than Imm	if $(R[rs1] < R[rs2])$ $PC = PC + \{imm, 1'b0\}$ (unsigned)	1100011	110	
	BGEU	BGEU	rs1, rs2, imm	SB	Branch if GE Imm	if $(R[rs1] \geq R[rs2])$ $PC = PC + \{imm, 1'b0\}$ (unsigned)	1100011	111	
Jump	JAL	JAL	rd, imm	UJ	Jump & Link	$R[rd] = PC + 4; PC = PC + \{imm, 1'b0\}$	1101111		
	JALR	JALR	rd, rs1, imm	UJ	Jump & Link Register	$R[rd] = PC + 4; PC = R[rs1] + imm$	1101111	000	


Datapath with Control

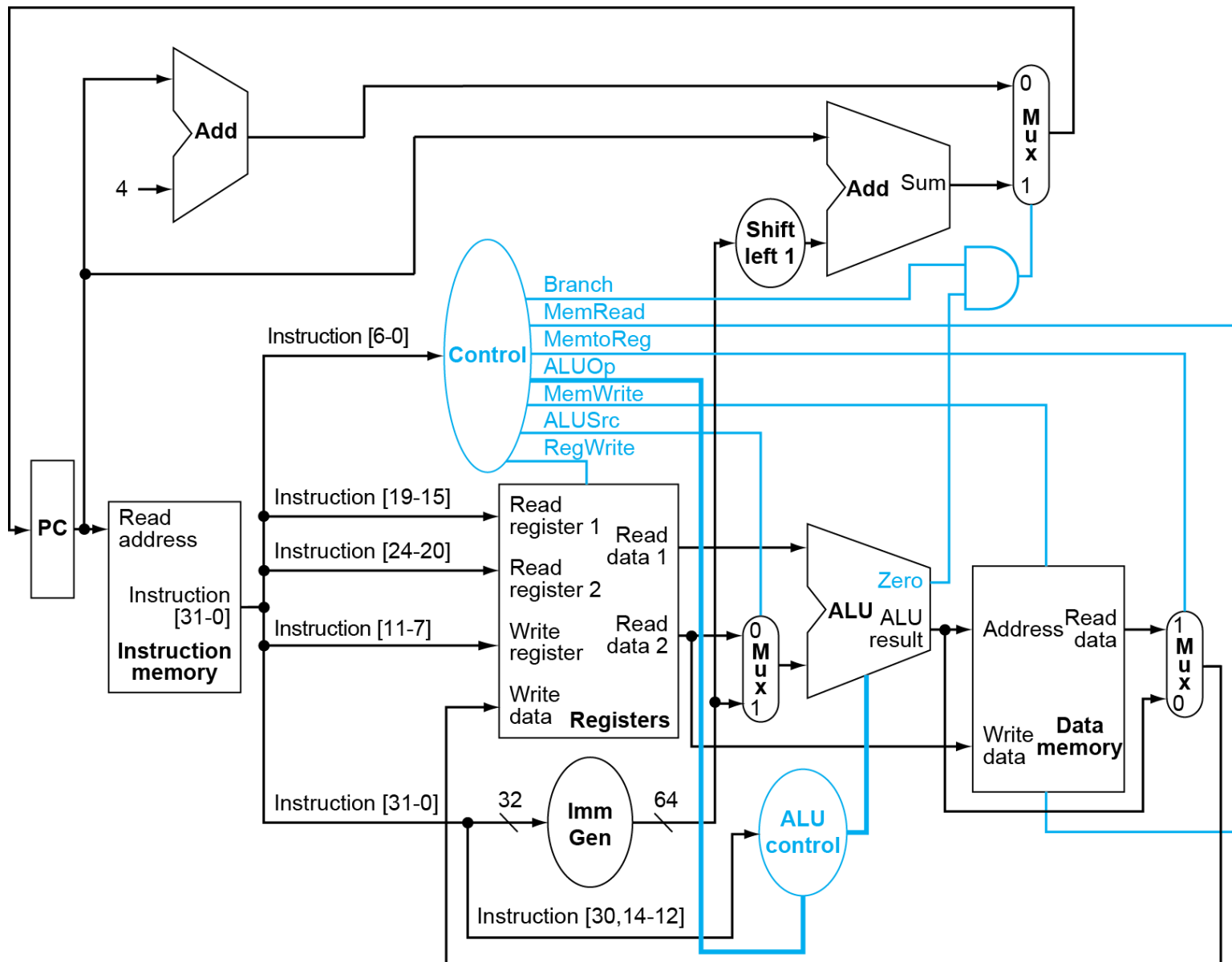


R-Type Instruction

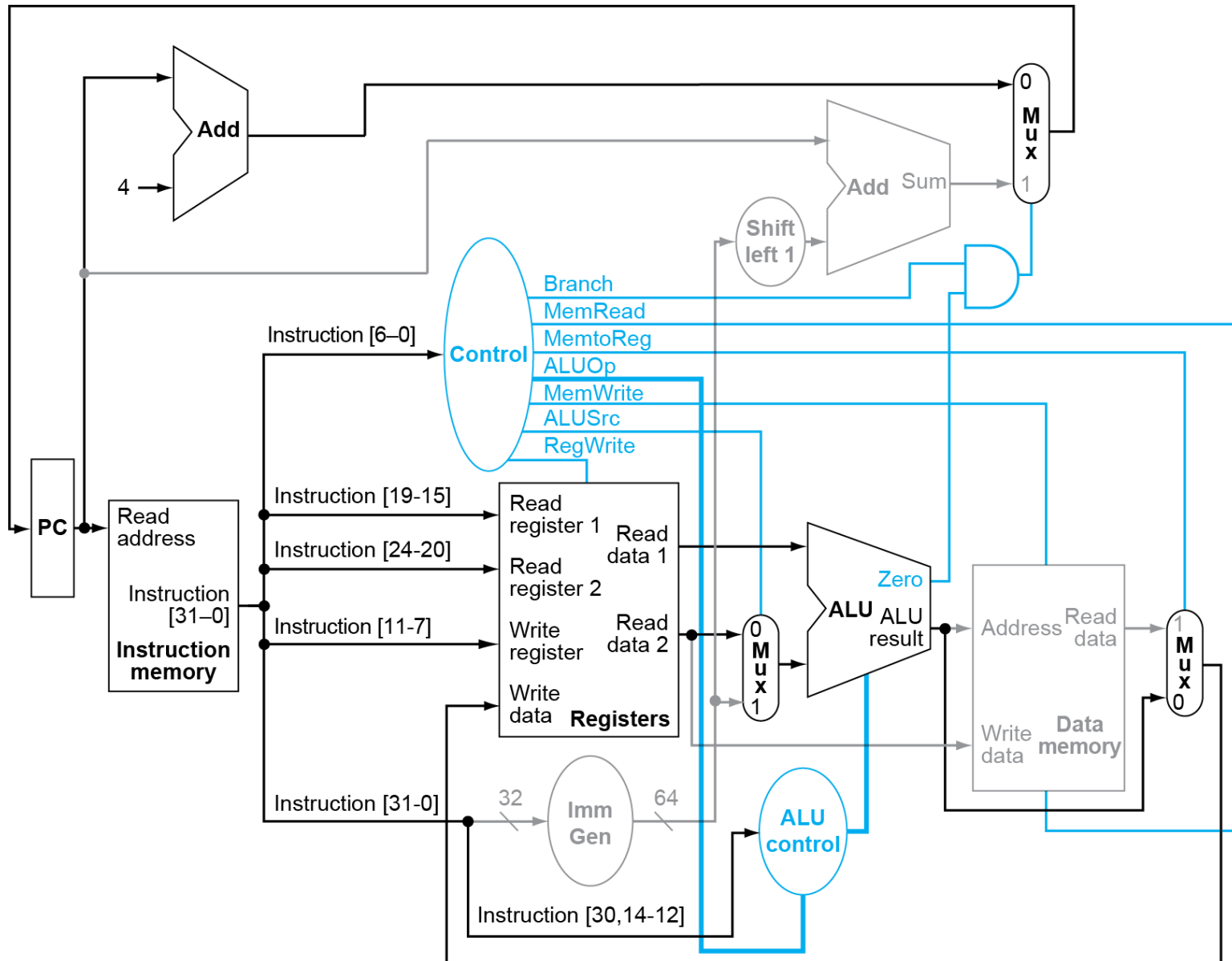

Load Instruction

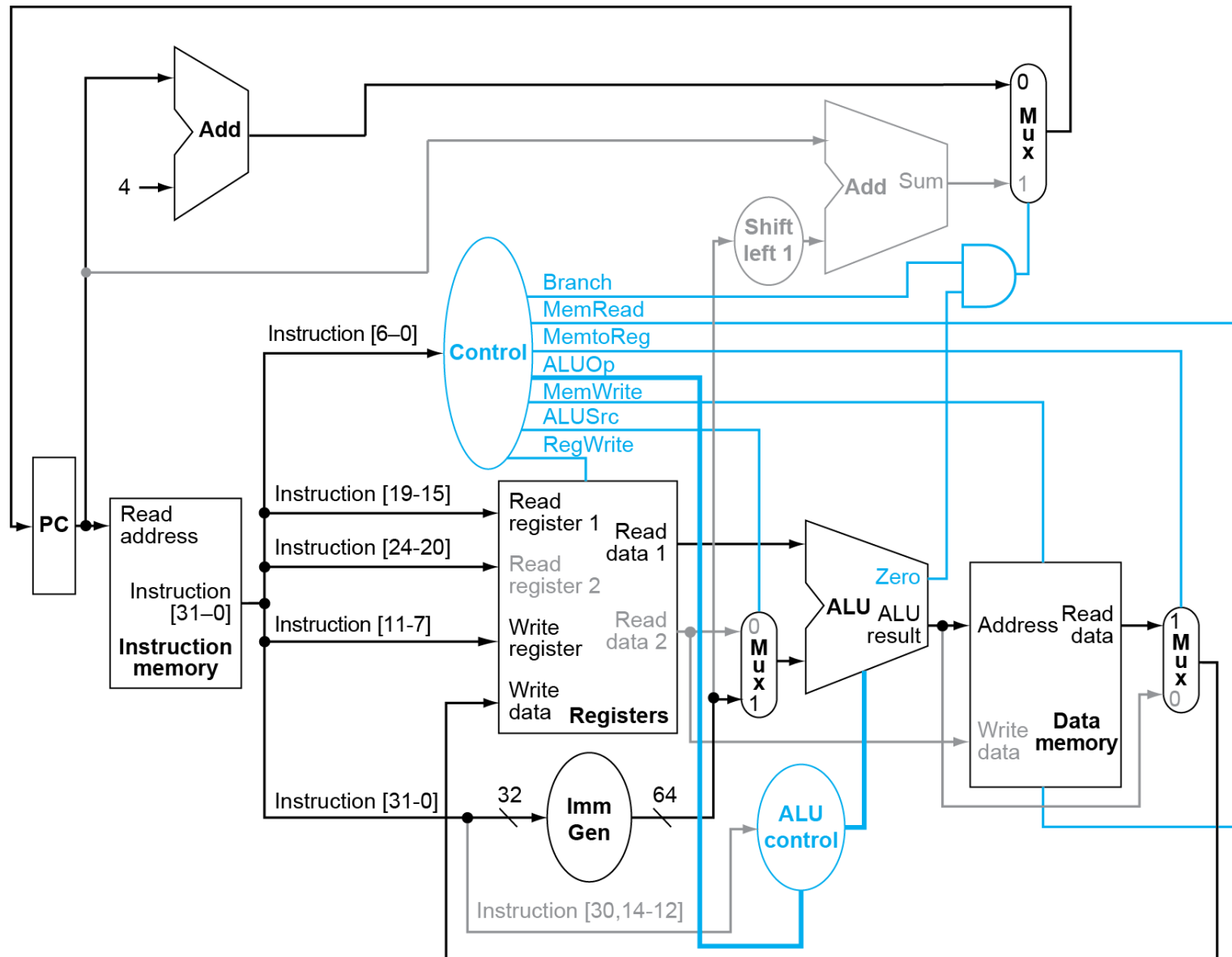

BEQ Instruction

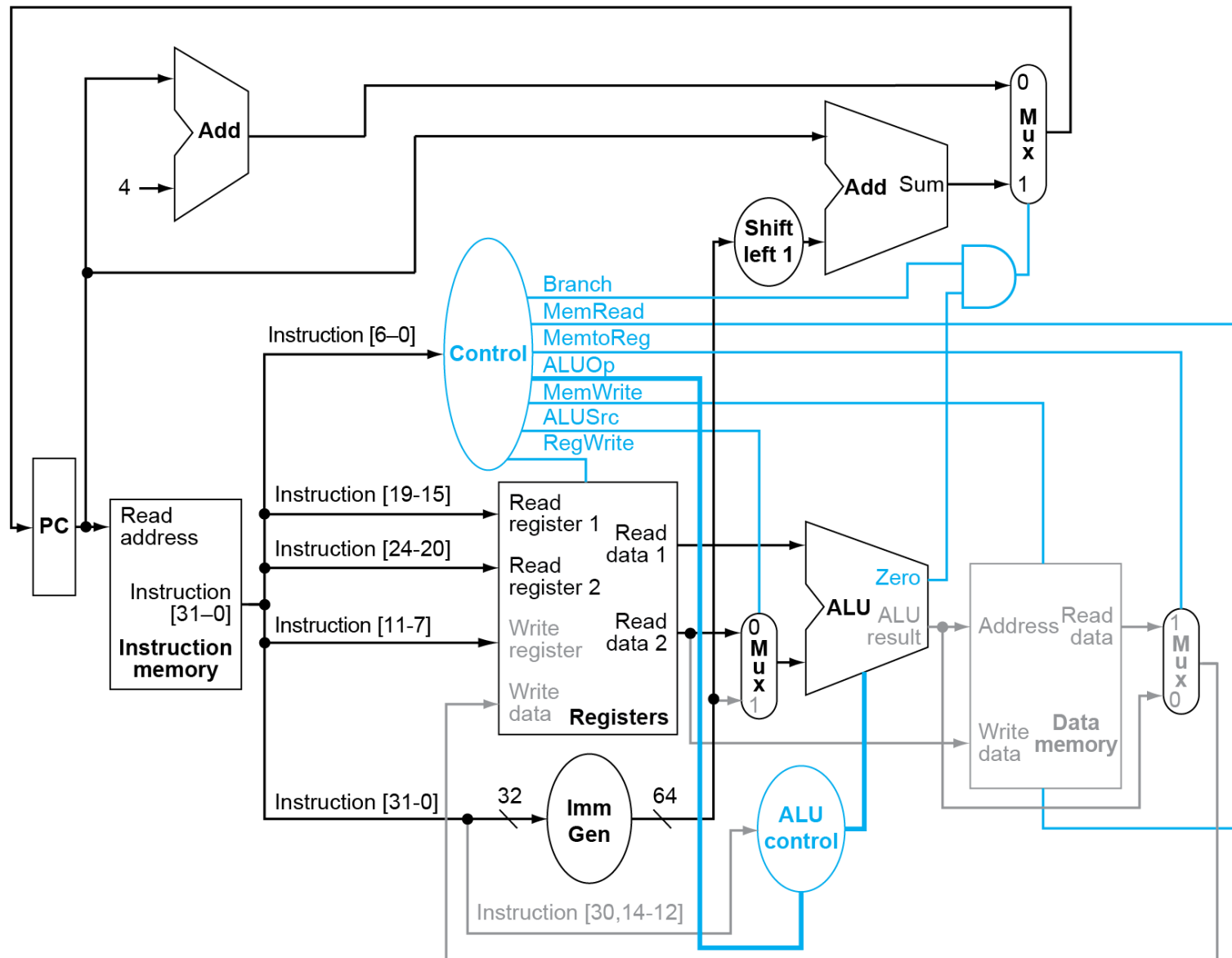

Performance Issues

- Longest delay determines clock period
 - Critical path: load instruction
 - Instruction memory → register file → ALU → data memory → register file
- Not feasible to vary period for different instructions
- Violates design principle
 - Making the common case fast
- We will improve performance by pipelining

Thank you

Questions?

Back-up Slides